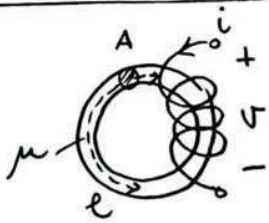


## LECTURE 13

### INDUCTORS & FIRST ORDER CIRCUITS




$$L = \frac{\mu N^2 A}{l}$$

$$\lambda = L \cdot i \quad \text{magnetic flux}$$

$$v_L = \frac{d\lambda}{dt} = L \cdot \frac{di}{dt}$$


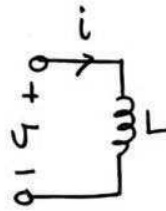
$$i = \frac{1}{L} \int_{-\infty}^t v(t) dt$$





Energy storage

$$p = v \cdot i = L \frac{di}{dt} i = \frac{d}{dt} \left( \frac{1}{2} L i^2 \right)$$

#### INDUCTOR & VOLTAGE SOURCE

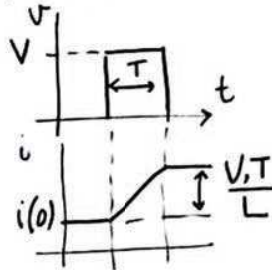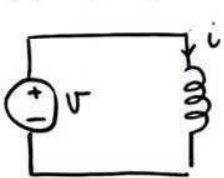



#### FIRST ORDER RL CIRCUIT

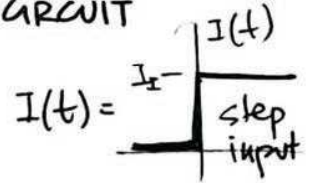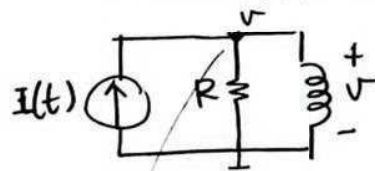

$$\text{node} \quad -I + \frac{v}{R} + i_L = 0$$





$$\frac{L}{R} \frac{di_L}{dt} + i_L = I_1$$
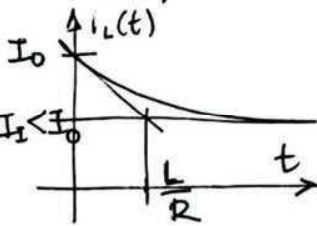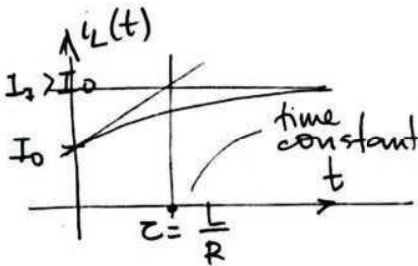
$$i_L = (I_0 - I_1) e^{-\frac{R}{L}t} + I_1 = I(0) \cdot e^{-\frac{R}{L}t} + I(+\infty)(1 - e^{-\frac{R}{L}t})$$



## LECTURE 14



### SPEED OF DIGITAL CIRCUITS

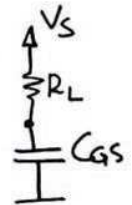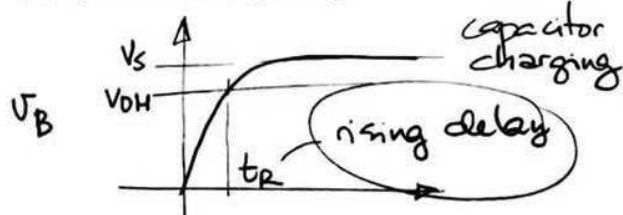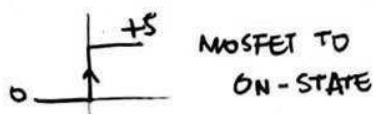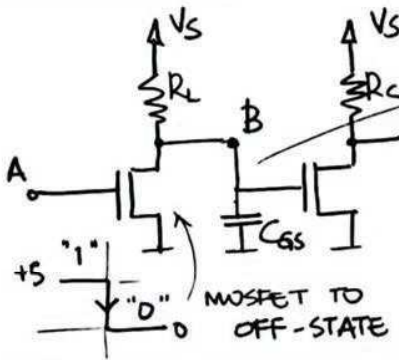

$$v_B = V_S \left( 1 - e^{-t/R_L C_{GS}} \right) \Big|_{t=t_r} = V_{OH} \quad t_r = -R_L C_{GS} \ln \left( 1 - \frac{V_{OH}}{V_S} \right)$$

ej. 0.16 ns ) similar C = 0.1 ns
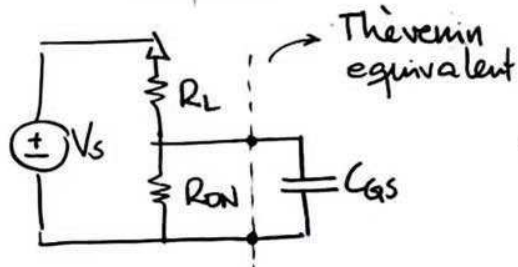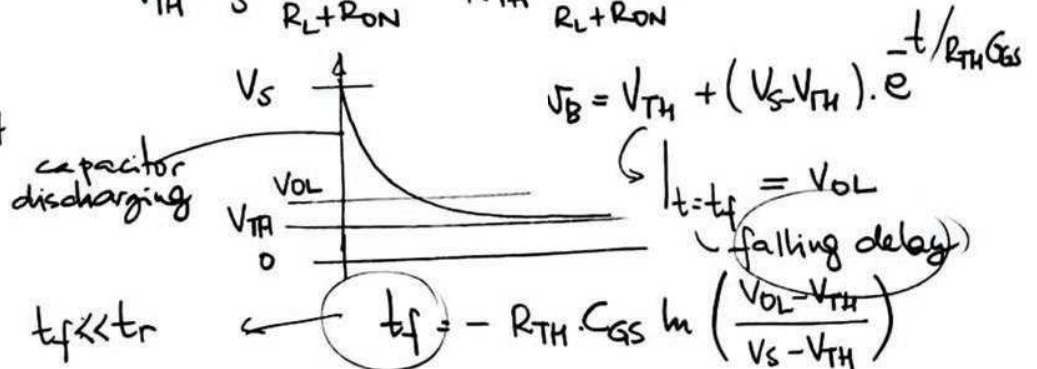
$$V_{TH} = V_S \frac{R_{ON}}{R_L + R_{ON}} \quad R_{TH} = \frac{R_{ON} R_L}{R_L + R_{ON}}$$



# LECTURE 15

## RAMPS, STEPS & IMPULSES

Notation for a step

Unit step

$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

Rising step

$$v(t) = V_I \cdot u(t)$$

Falling step



$$v(t) = V_I(1 - u(t))$$

Time translated step

$$v(t) = V_I(u(t - T))$$

Response to STEP INPUT



RC circuit. Thevenin form

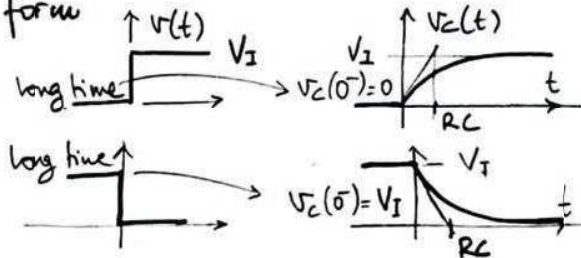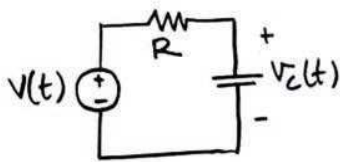

ZERO STATE RESPONSE  
 $v_C(t) = V_I(1 - e^{-t/RC})$

$$v_C(t) = V_I \cdot e^{-t/RC}$$



RC circuit. Norton form

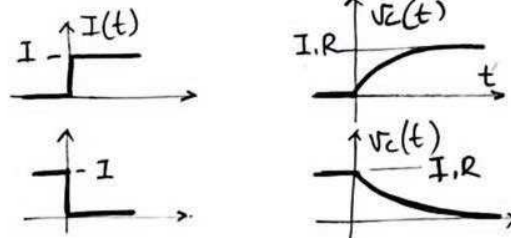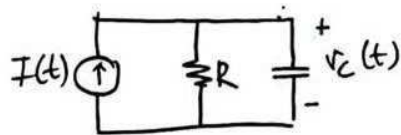

$$v_C(t) = I \cdot R(1 - e^{-t/RC})$$

$$v_C(t) = I \cdot R e^{-t/RC}$$


RL circuit. Norton form

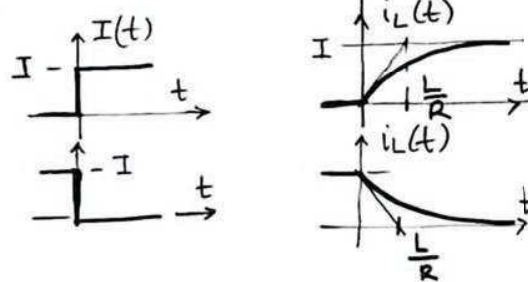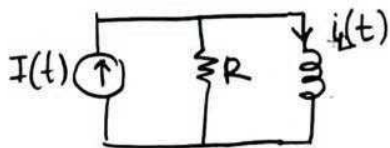



$$i_L(t) = I(1 - e^{-tR/L})$$

$$i_L(t) = I e^{-tR/L}$$


RC circuit response to PULSE INPUT

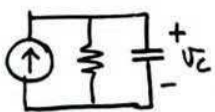





LONG PULSE  $T \gg RC$

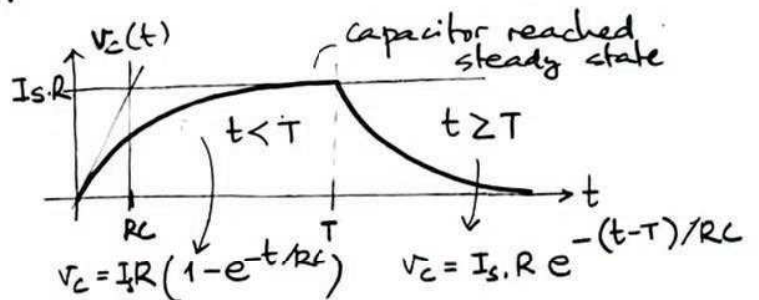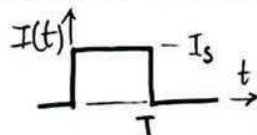




SHORT PULSE

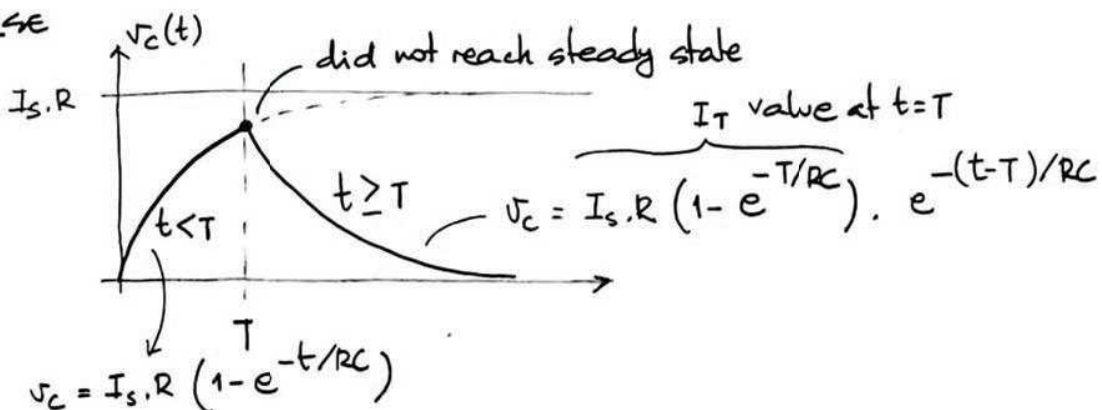

## RC circuit response to IMPULSE input

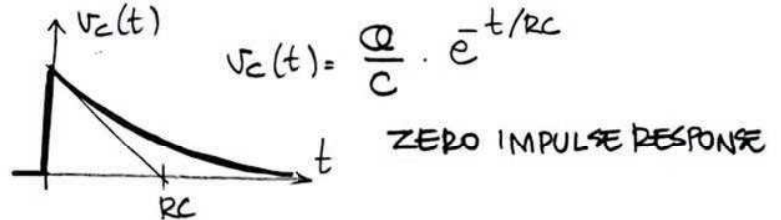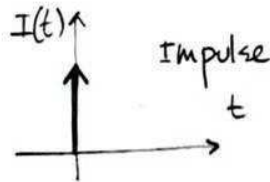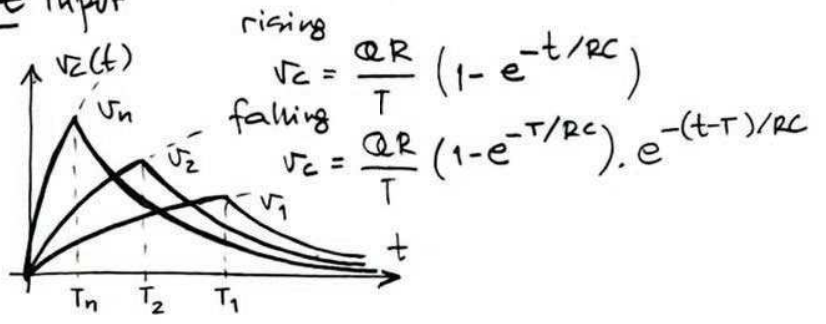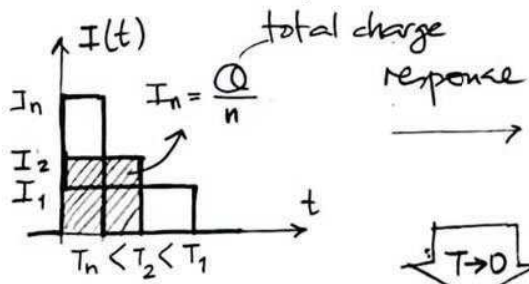



## RL circuit response to IMPULSE input

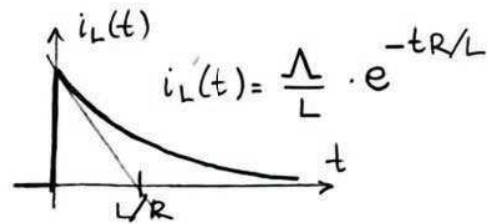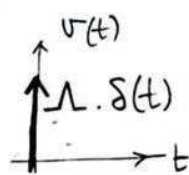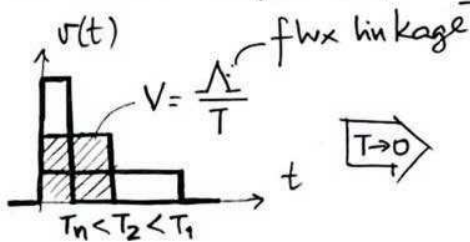

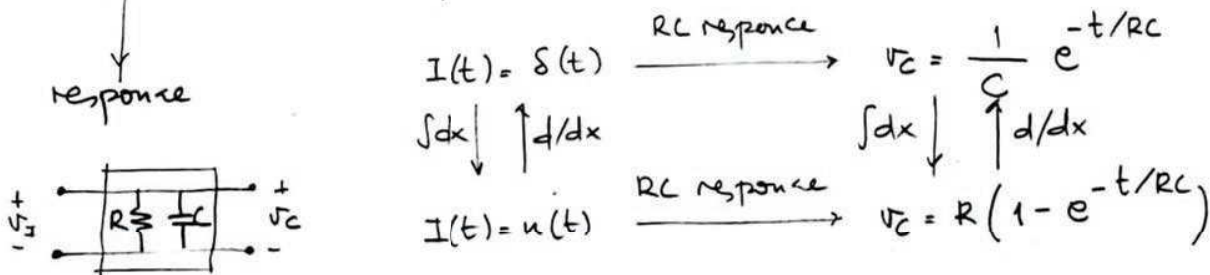
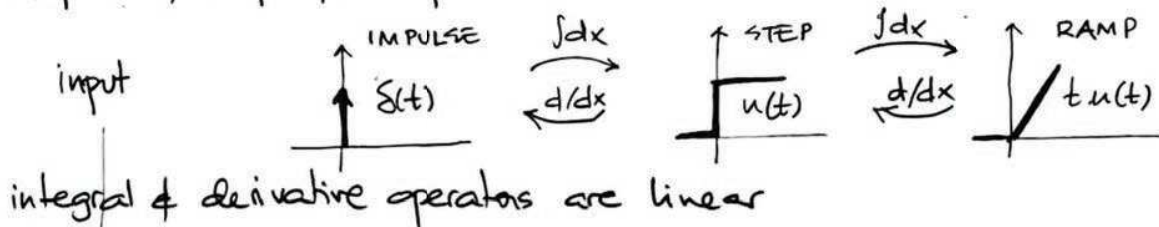
## Superposition with initial conditions & source

- Treat initial conditions as sources
- Find response to each source

Impulses, steps & Ramps: No source, No initial conditions  $\rightarrow$  LINEAR SYSTEMS




## CROSSTALK BETWEEN TWO CIRCUITS

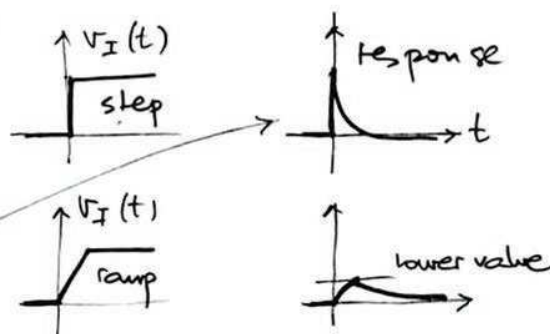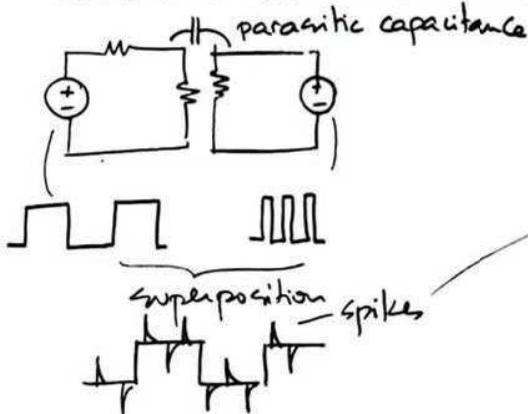




# LECTURE 16



## STATE & MEMORY

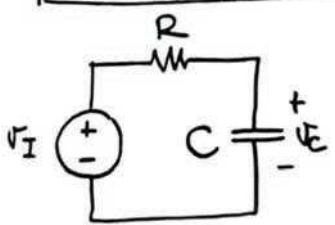

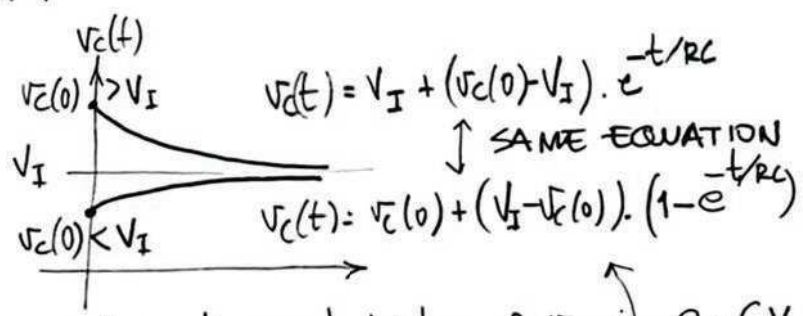$v_I(t) = V_I$  for  $t \geq 0$   
 $v_I(t)$  for  $t < 0$





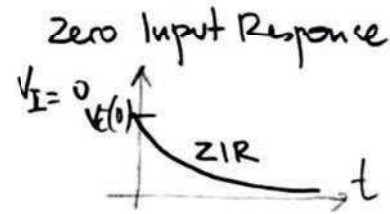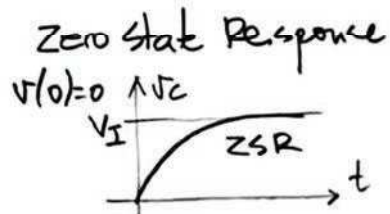$v_C = f(v_C(0), v_I)$      $v_C(0)$  - state, captures the past history of  $v_I$  in  $q = CV$   
 $v_I(t)$  - input    SAME EQUATION




Total Response  
 $v_C(t) = V_0 \cdot e^{-t/RC} + V_I(1 - e^{-t/RC})$   
 $v_C(t) = ZIR + ZSR$


### Digital Memory Abstraction

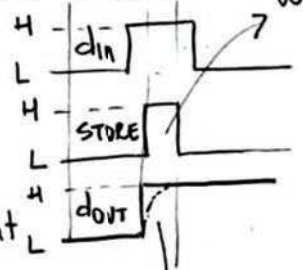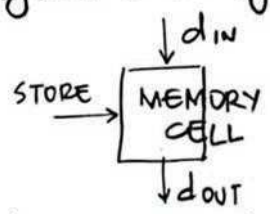

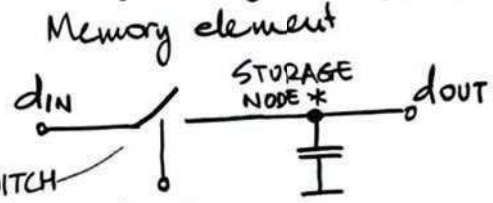
when 'store' goes high, output follows input



### Building a Memory Element


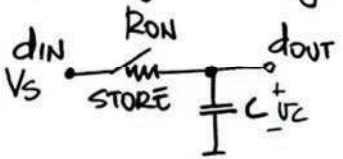


real switch with  $R_{ON}$

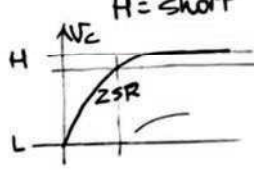


$V_{OH} = V_S(1 - e^{-t/R_{ON}C})$   
 $T_{pulse} \gg T_{min}$  minimum store pulse to reach  $V_{OH}$



### Storage Time

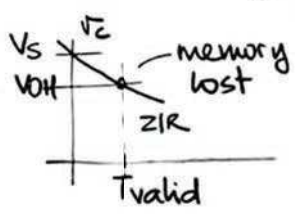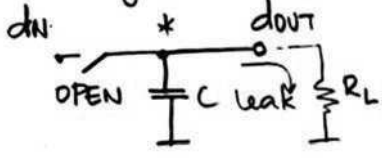


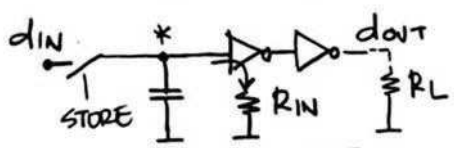
$V_{OH} = V_S \cdot e^{-t/R_L C}$   
 $T_{valid} = -R_L C \ln \frac{V_{OH}}{V_S}$  → THIS DOES NOT WORK!  
 THE CIRCUIT IS BETTER



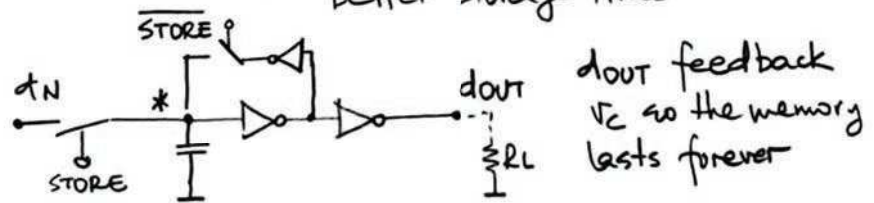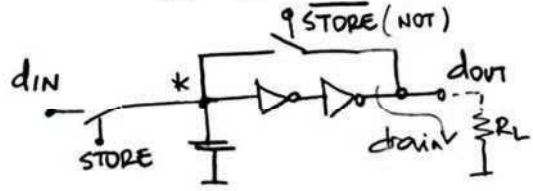$T_{valid} = -R_{IN} C \ln \frac{V_{OH}}{V_S}$   
 $R_{IN} \gg R_L$  ~ in the order of 1 ms better storage time




### Four bit memory array

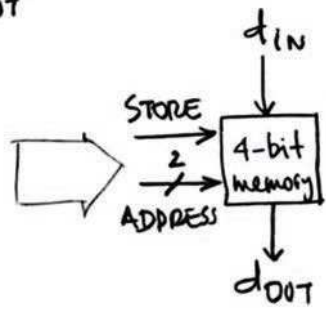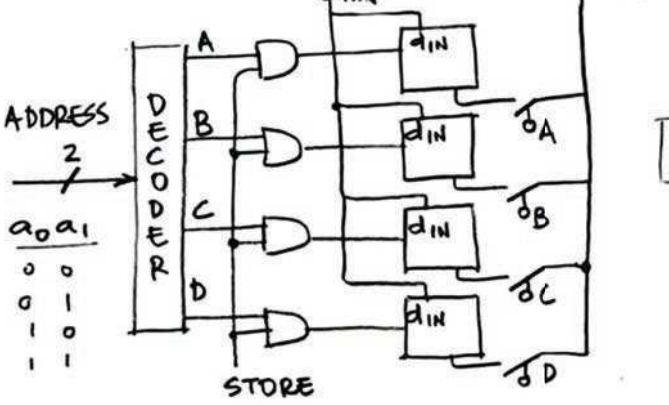



# LECTURE 17

## UNDAMPED SECOND-ORDER SYSTEMS

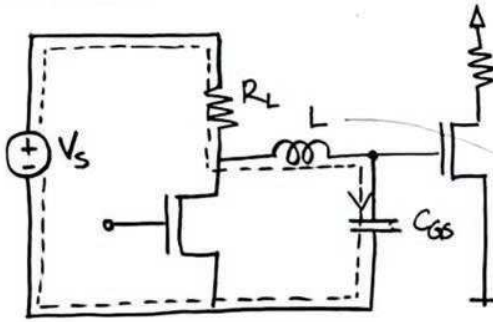

-->--  
current loop with  
some inductance  
modelled by a  
lumped inductor L

SECOND-ORDER CIRCUIT

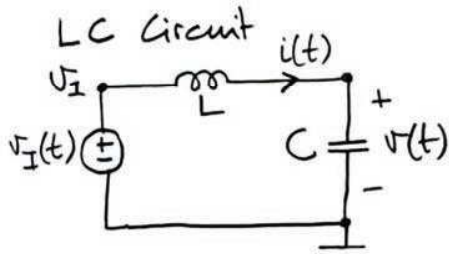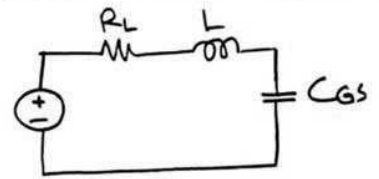

$$i(t) = C \frac{dv}{dt}$$

$$V_I - v = LC \frac{d^2v}{dt^2} \quad \text{units time}^2$$

$$V_I - v = L \frac{di}{dt}$$

$$LC \frac{d^2v}{dt^2} + v = V_I \quad \text{LC differential equation}$$

Input step  $V_I$   $\uparrow$   $v_I(t)$

Initial conditions  $v(0) = 0 \quad i(0) = 0$

ZERO STATE RESPONSE

Differential eq. solution = PARTICULAR + HOMOGENEOUS = TOTAL solution

Particular solution  $v_p(t) = V_I$

Homogeneous solution

$$LC \frac{d^2v_H}{dt^2} + v_H = 0$$

$$v_H = A \cdot e^{st}$$

$$LCAs^2 e^{st} + A e^{st} = 0$$

$$LCs^2 + 1 = 0 \quad \text{characteristic equation}$$

$$s = \pm j\omega_0$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$


Total solution with initial conditions (ZSR)

$$v(t) = V_I + A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t} \quad \left| \begin{array}{l} v(0) = V_I + A_1 + A_2 = 0 \\ i(0) = A_1 C j\omega_0 - A_2 C j\omega_0 = 0 \end{array} \right. \quad \left\{ \begin{array}{l} A_1 = A_2 = -\frac{V_I}{2} \end{array} \right.$$

$$i(t) = A_1 C j\omega_0 e^{j\omega_0 t} - A_2 C j\omega_0 e^{-j\omega_0 t}$$

$$v(t) = V_I - V_I \left( \frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2} \right) = V_I - V_I \cos \omega_0 t$$
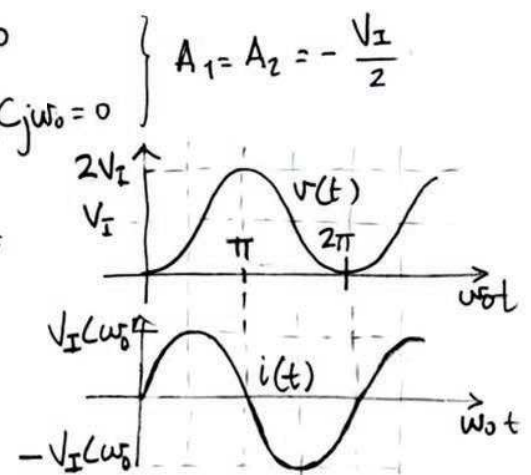
$$i(t) = -V_I C \omega_0 \left( \frac{e^{j\omega_0 t} - e^{-j\omega_0 t}}{2} \right) = V_I C \omega_0 \sin \omega_0 t$$



Zero Input  $v_I(t) = 0$  Initial conditions  $v(0) = V; i(0) = 0$

$$LC \frac{d^2v}{dt^2} + v = 0 \quad v(t) = A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$$


$$v(0) = A_1 + A_2 = V$$

$$i(0) = CA_1 j\omega_0 - CA_2 j\omega_0 = 0$$

$$\left\{ \begin{array}{l} A_1 = A_2 = \frac{V}{2} \end{array} \right.$$


$$v(t) = V \left( \frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2} \right) = V \cos \omega_0 t$$
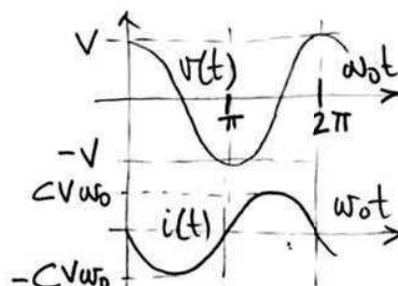
$$i(t) = C \frac{dv}{dt} = -CV \omega_0 \sin \omega_0 t$$



ENERGY


$$E_L + E_C = \text{const.}$$

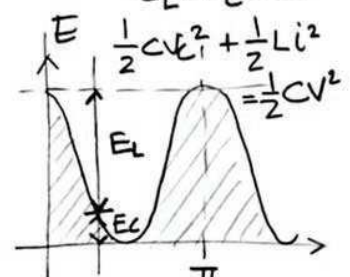



# LECTURE 18

## DAMPED SECOND-ORDER SYSTEMS

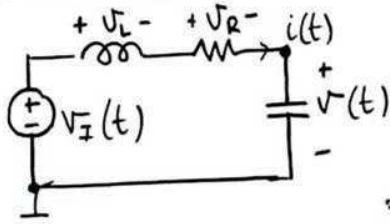

$$i = C \frac{dv}{dt} \quad v_R = R \cdot i = RC \frac{dv}{dt} \quad v_L = L \frac{di}{dt} = LC \frac{d^2v}{dt^2}$$

$$v_I(t) = v_L + v_R + v_C = LC \frac{d^2v}{dt^2} + RC \frac{dv}{dt} + v \rightarrow \text{constant coefficient ODE}$$

ZERO STATE RESPONSE  $v_I = V_I \cdot u(t) \Rightarrow v(0) = 0 \quad i(0) = 0$

ODE Particular solution

$$LC \frac{d^2v_p}{dt^2} + RC \frac{dv_p}{dt} + v_p = V_I(t) \Rightarrow v_p = V_I \quad t \geq 0$$

ODE Homogeneous solution

$$\frac{d^2v_h}{dt^2} + \frac{R}{L} \frac{dv_h}{dt} + \frac{1}{LC} v_h = 0$$

Solution trial

Characteristic Eq.

Canonic form



$$v_h = A \cdot e^{st} \Rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \Rightarrow s^2 + 2\alpha s + \omega_0^2 = 0 \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \alpha = \frac{R}{2L} \Rightarrow$$

Roots

$$\Rightarrow s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \Rightarrow \text{ODE total solution } v(t) = V_I + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

OVERDAMPED CASE  $\alpha > \omega_0 \quad s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -\alpha_1 \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -\alpha_2$
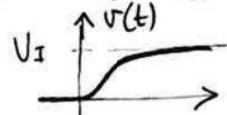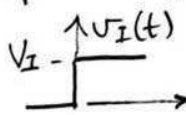
$$v(t) = V_I + A_1 e^{-\alpha_1 t} + A_2 e^{-\alpha_2 t}$$




UNDERDAMPED CASE  $\alpha < \omega_0 \quad \sqrt{\alpha^2 - \omega_0^2} = j\sqrt{\omega_0^2 - \alpha^2} = j\omega_d$  damped natural freq.


$$v(t) = V_I + A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t} = V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t =$$

$$= V_I + A e^{-\alpha t} \cos(\omega_d t + \phi)$$
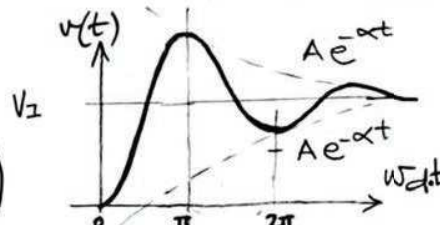
$$A = -V_I \frac{\omega_0}{\omega_d} \quad \phi = -\arctan\left(\frac{\alpha}{\omega_d}\right)$$



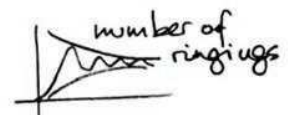
$$Q = \frac{\omega_0}{2\alpha} = \text{Quality factor}$$



CRITICALLY DAMPED CASE  $\alpha = \omega_0 \quad s_1 = s_2 = -\alpha$




INTUITIVE ANALYSIS

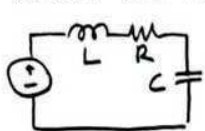


$$\omega_0 = \sqrt{1/LC}$$

$$\alpha = R/2L$$
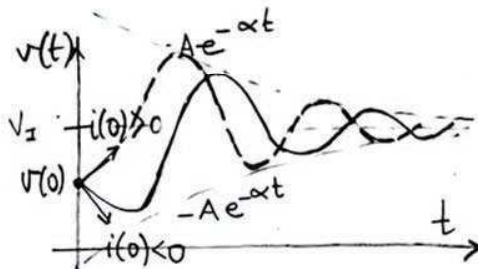
$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$



PARALLEL RLC CIRCUIT

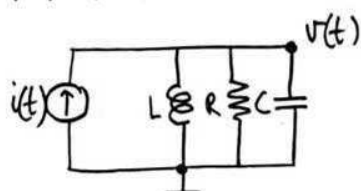


$$i(t) = i_L + i_R + i_C = \frac{1}{L} \int_{-\infty}^t v dt + \frac{v}{R} + C \frac{dv}{dt} \Rightarrow \frac{1}{C} \frac{d}{dt}$$

Homogeneous solution

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0 \Rightarrow \omega_0 = \sqrt{\frac{1}{LC}} \quad \alpha = \frac{1}{2RC} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

# LECTURE 19

## SINUSOIDAL STEADY STATE

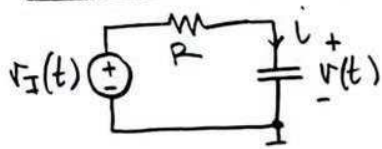

$$v_I(t) = \begin{cases} V_i \cos \omega t & t \geq 0 \\ 0 & t < 0 \end{cases}$$

$v(0) = 0$  Zero State Response

Fourier analysis:

Any signal can be expressed as a sum of sinusoids.

Sinusoidal response of RC network. ODE:  $RC \frac{dv}{dt} + v = v_I$

Particular solution: Trigonometric approach

$$a \sin \alpha + b \cos \alpha = \sqrt{a^2 + b^2} \cos(\alpha + \phi)$$

$$v_p = A \cos(\omega t + \phi) \quad -RC A \omega \sin(\omega t + \phi) + A \cos(\omega t + \phi) = V_i \cos \omega t \quad \phi = -\arctan \frac{b}{a}$$

$$A = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \quad \phi = -\arctan(\omega RC)$$

Particular solution: Exponential approach  $v_{Is} = V_i e^{st} = V_i e^{j\omega t} \quad v_I = \text{Re}[v_{Is}]$

$$v_{ps} = A e^{st} \quad RC A s e^{st} + A e^{st} = V_i e^{st} \quad A = \frac{V_i}{sRC + 1} = \frac{V_i}{1 + j\omega RC} \text{ complex amplitude}$$


$$v_p = \text{Re}[v_{ps}] = \text{Re}\left[\frac{V_i}{1 + j\omega RC} e^{j\omega t}\right] = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi) \quad \phi = -\arctan(\omega RC)$$

Homogeneous solution

$$RC \frac{dv_H}{dt} + v_H = 0 \quad v_H = A \cdot e^{-t/RC}$$

Total solution & initial conditions
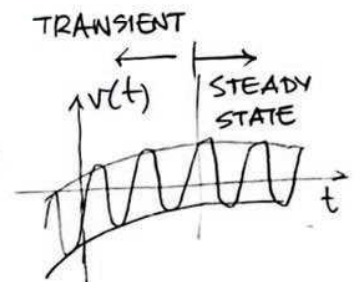
$$v(t) = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi) - \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos \phi e^{-t/RC}$$





SINUSOIDAL STEADY STATE  $t \gg RC \rightarrow v_H = 0 \quad v(t) = v_p$

$$v(t) = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi) \quad \phi = -\arctan(\omega RC) \quad v_p = |V_p| \cos(\omega t + \angle V_p)$$

MAGNITUDE & PHASE PLOTS: TRANSFER FUNCTIONS

$$H(j\omega) = \frac{V_p}{V_i} \quad |H(j\omega)| = \left|\frac{V_p}{V_i}\right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$
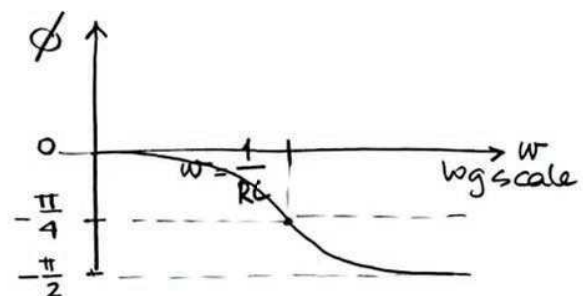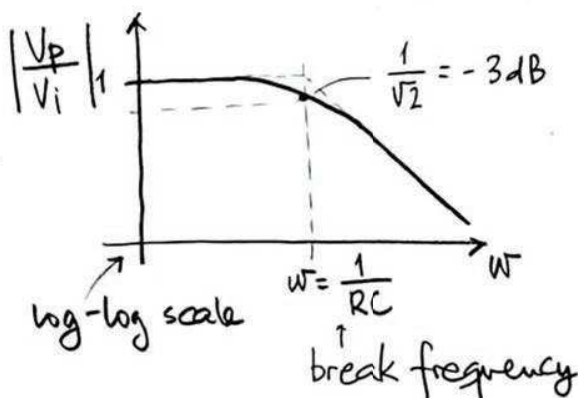
$$\angle H(j\omega) = \phi = -\arctan(\omega RC)$$





# LECTURE 20


## THE IMPEDANCE MODEL

$$i = I \cdot e^{st}$$

$$v = V \cdot e^{st}$$

$$s = j\omega$$


IMPEDANCE

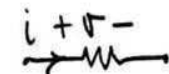

$$v = i \cdot R$$

$$V_R \cdot e^{st} = I_R \cdot e^{st} \cdot R$$

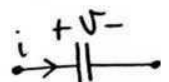
$$V_R = R \cdot I_R \quad \text{complex amplitudes of } V, I$$



$$i = C \cdot \frac{dv}{dt}$$

$$I_C \cdot e^{st} = C \cdot V_C \cdot s e^{st}$$


$$V_C = \frac{1}{sC} \cdot I_C$$

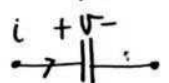

$$v = L \cdot \frac{di}{dt}$$

$$V_L \cdot e^{st} = L \cdot I_L \cdot s e^{st}$$

$$V_L = sL \cdot I_L$$

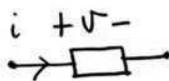


$$V = Z \cdot I \quad \text{generalized Ohm's Law}$$

$$Z_R = R \quad \left| \quad Z_C = \frac{1}{sC} = \frac{1}{j\omega C} = \frac{-j}{\omega C} \quad \right| \quad Z_L = sL = j\omega L$$

### IMPEDANCE METHOD SUMMARY

1. Replace sources by their complex amplitudes
2. Replace circuit elements by their impedances (topology REMAINS!)
3. Solve circuit with the 5 circuit analysis methods
4. Obtain the time domain variables (not always)  $v_a = |V_a| \cos(\omega t + \angle V_a)$

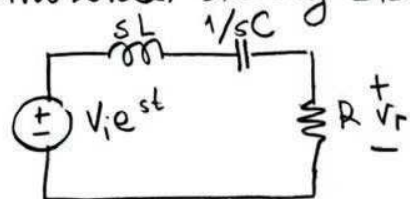Sinusoidal steady-state (SSS) response of series RLC network



$$V_r = V_i \cdot \frac{R}{R + sL + \frac{1}{sC}}$$

$$= \frac{V_i \cdot sR/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

RLC series characteristic equation


Frequency response of RLC series circuit  $s = j\omega$

$$\frac{V_r}{V_i} = \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC}$$

$$\left| \frac{V_r}{V_i} \right| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}}$$

Amplitude plot


$$\text{Low } \omega \quad \left| \frac{V_r}{V_i} \right| \approx \omega RC \quad \text{High } \omega \quad \left| \frac{V_r}{V_i} \right| \approx \frac{R}{\omega L} \quad \omega = \frac{1}{\sqrt{LC}} \quad \left| \frac{V_r}{V_i} \right| = 1$$

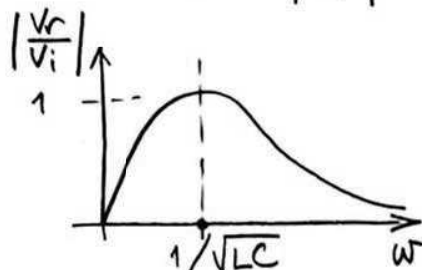






















# LECTURE 21

## FILTERS

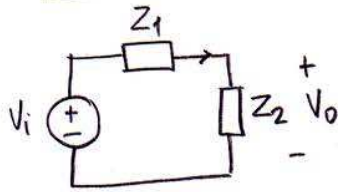

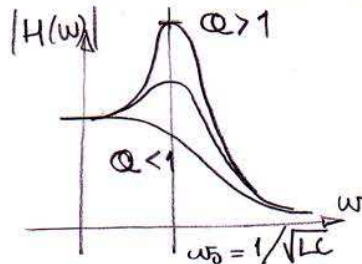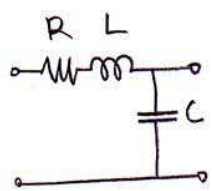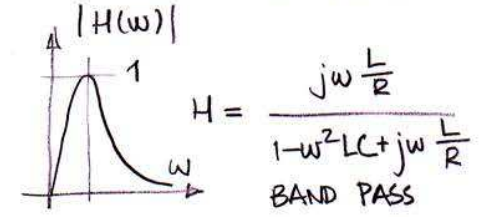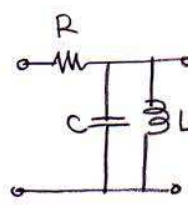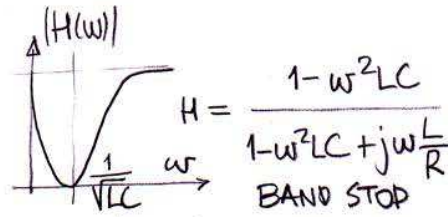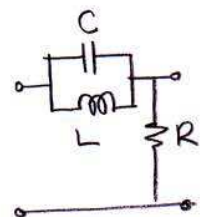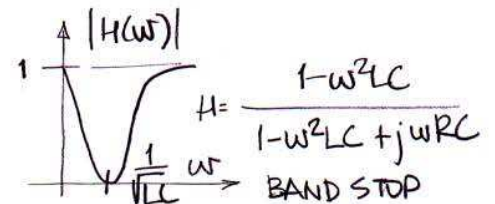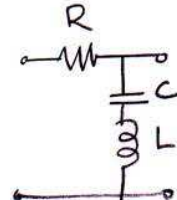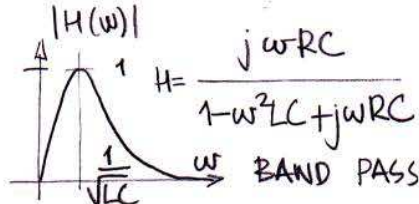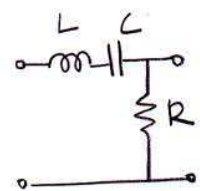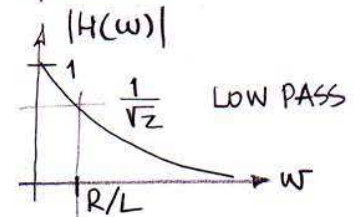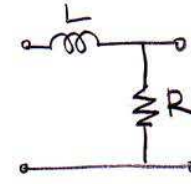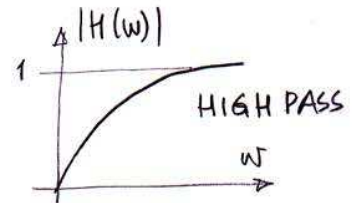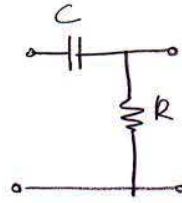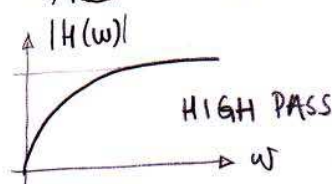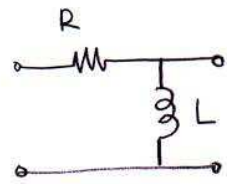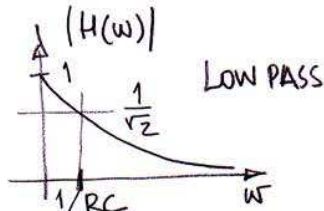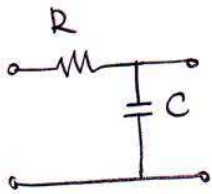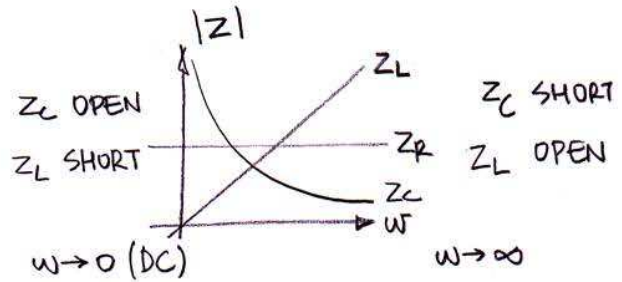
$$H(\omega) = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2}$$



$$H = \frac{1}{1 - \omega^2 LC + j\omega RC} = \frac{\omega_0}{\omega_0^2 - \omega^2 + j2\alpha}$$

$$|H(\omega_0)| = Q = \frac{\omega_0}{2\alpha} \quad \text{Resonance Quality factor}$$

### SELECTIVITY & Q-FACTOR

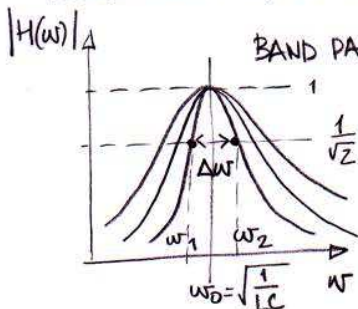

$$Q = \frac{\omega_0}{\Delta\omega}$$

bandwidth for  $|H| = \frac{1}{\sqrt{2}}$  (half power)

$$\frac{\omega L}{R} - \frac{1}{\omega RC} = \pm 1$$


$$\omega_{1,2} = \pm \frac{R}{2L} + \frac{1}{2} \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}$$

$$\Delta\omega = \frac{R}{L} = 2\alpha$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

for series RLC


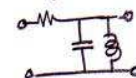
$$\frac{1}{RC} = 2\alpha \text{ for parallel RLC}$$




# LECTURE 22

## TIME DOMAIN VS. FREQUENCY DOMAIN ANALYSIS


Different filters in the same circuit

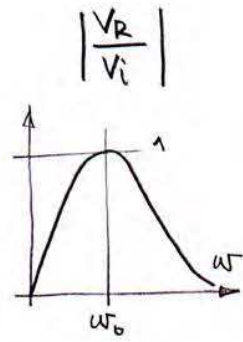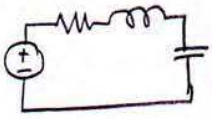


BAND PASS

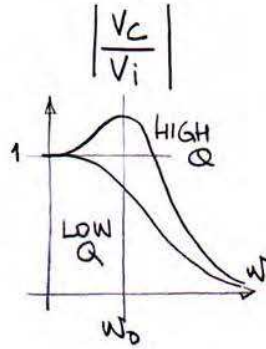

LOW PASS

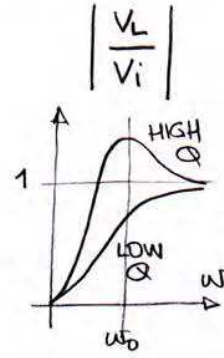


HIGH PASS

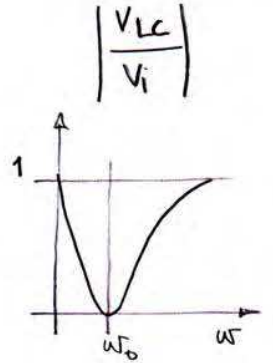

BAND STOP



Comparison (Apple & Orange)

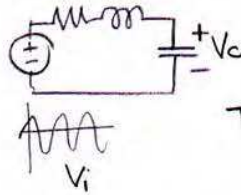



FREQUENCY ANALYSIS

TIME ANALYSIS

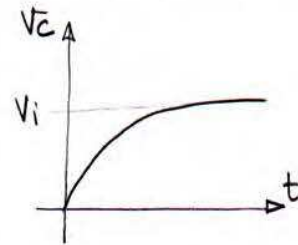
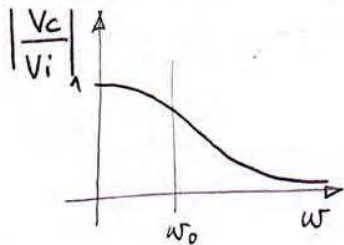
$\alpha > \omega_0$   
 $Q < \frac{1}{2}$   
 overdamped



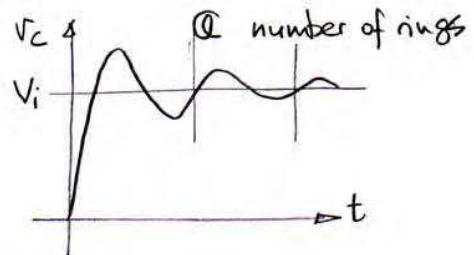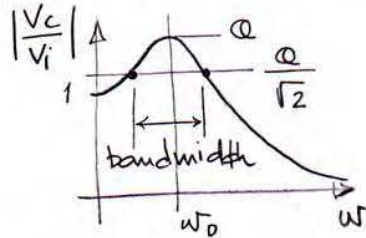$\alpha < \omega_0$   
 $Q > \frac{1}{2}$   
 underdamped



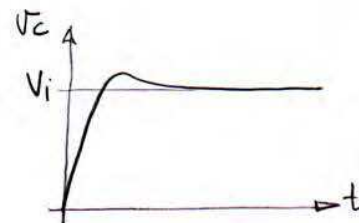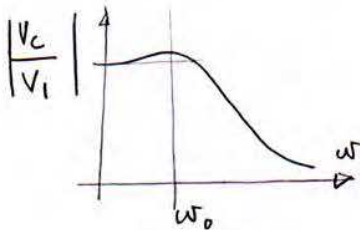
$\alpha = \omega_0$   
 $Q = \frac{1}{2}$   
 critically damped





## LECTURE 23


## THE OPERATIONAL AMPLIFIER ABSTRACTION

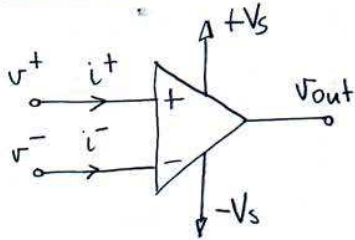

IDEAL OP-AMP

$$\begin{aligned} R_{out} &\rightarrow 0 \\ R_{in} &\rightarrow +\infty \\ A &\rightarrow \infty \\ \text{no saturation} \end{aligned}$$

Noninverting amplifier

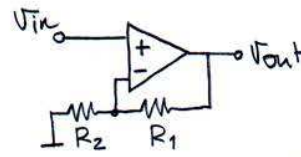


$$\begin{aligned} v_{out} &= A(v^+ - v^-) \\ v^+ &= v_{in} \quad v^- = v_{out} \frac{R_2}{R_1 + R_2} \end{aligned}$$

$$v_{out} = \frac{A v_{in}}{1 + \frac{AR_2}{R_1 + R_2}} \stackrel{A \gg 1}{\approx} \frac{R_1 + R_2}{R_2} v_{in}$$


Negative feedback: Virtual short method

$$i^+ \approx 0 \quad i^- \approx 0 \quad v^+ \approx v^-$$

Voltage follower

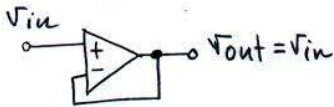

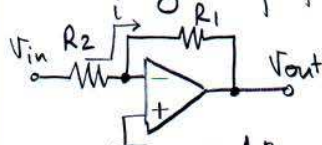Inverting amplifier: virtual ground  $v^- = v^+ = 0$



$$\frac{v_{in}}{R_2} = i = -\frac{v_{out}}{R_1} \quad v_{out} = -\frac{R_1}{R_2} v_{in}$$


$$v_{out} = \frac{-AR_1}{R_1 + R_2 + AR_2} v_{in}$$

$$\begin{aligned} \text{Input resistance: } R_{in} &= R_2 \\ R_{in} &= \frac{R_1 + R_2 + AR_2}{1 + A} \end{aligned}$$

## LECTURE 24

## OPERATIONAL AMPLIFIER CIRCUITS

Differential amplifier

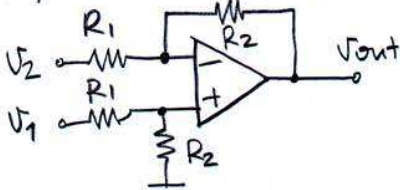


$$\begin{aligned} v^+ &= v_1 \frac{R_2}{R_1 + R_2} \\ \frac{v_2 - v^-}{R_1} + \frac{v_{out} - v^-}{R_2} &= 0 \end{aligned}$$

$$v^- = \frac{v_2 R_2 + v_{out} R_1}{R_1 + R_2} = v^+ = \frac{R_2}{R_1 + R_2} v_1$$


$$v_{out} = \frac{R_2}{R_1} (v_1 - v_2)$$

Integrator

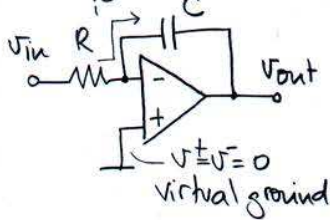


$$\begin{aligned} \frac{v_{in}}{R} = i &= -C \frac{dv_{out}}{dt} \\ v_{out} &= \frac{-1}{RC} \int_{-\infty}^t v_{in} dt \end{aligned}$$

Differentiator

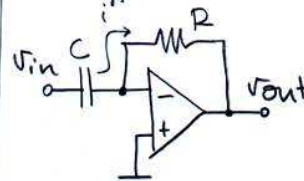


$$\begin{aligned} C \frac{dv_{in}}{dt} = i &= -\frac{v_{out}}{R} \\ v_{out} &= -RC \frac{dv_{in}}{dt} \end{aligned}$$

Op-Amp Filters: Impedance model

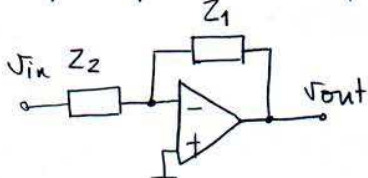

$$v_{out} = -\frac{Z_1}{Z_2} v_{in}$$


Summing Amp

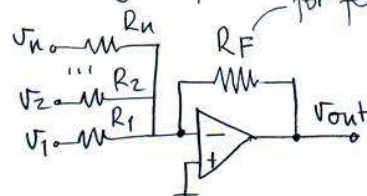

$$v_{out} = -R_f \left( \frac{v_1}{R_1} + \dots + \frac{v_n}{R_n} \right)$$


Non-linear Op-Amp circuits

Exponential Op-Amp

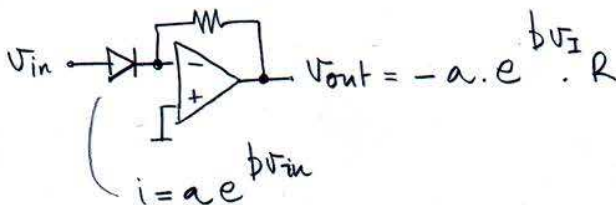

$$v_{out} = -a \cdot e^{b v_{in}} \cdot R$$

Log Op-Amp


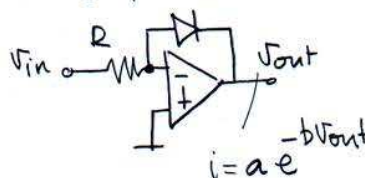


$$v_{out} = -\frac{1}{b} \ln \frac{v_{in}}{aR}$$

# LECTURE 26

## ENERGY & POWER




### MOSFET STATIC POWER

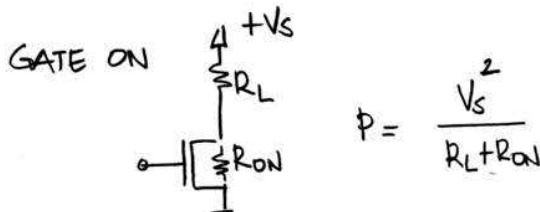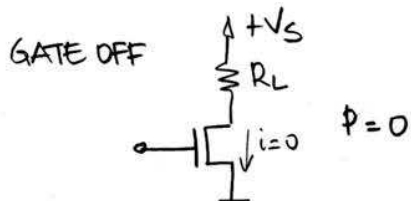

In a circuit with N mosfet, half will be on and half will be off (statistics)  
Expected power  $P = \frac{V_s^2}{2R_L}$   $R_L \gg R_{ON}$
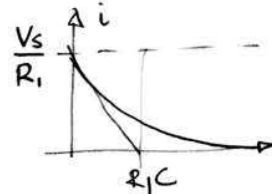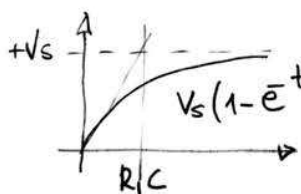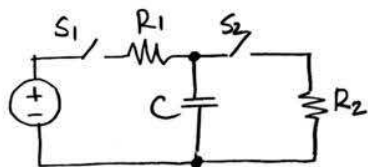
### MOSFET DYNAMIC POWER

$S_1$  short,  $S_2$  open  $t = [0, T_1]$




$$E_1 = \int_0^{T_1} P dt = \int_0^{T_1} V_s \cdot i dt = \frac{V_s^2}{R_1} \int_0^{T_1} (1 - e^{-t/RC}) dt = CV_s^2 (1 - e^{-T_1/RC}) \quad RC = \tau$$

$T_1 \gg RC$  then  $E_1 = CV_s^2$   $\left\{ \begin{array}{l} \frac{1}{2} CV_s^2 \text{ stored in } C \\ \frac{1}{2} CV_s^2 \text{ dissipated in } R_1 \text{ (independent of } R_1!) \end{array} \right.$

$S_1$  open,  $S_2$  short  $t = [T_1, T_1 + T_2]$

$T_2 \gg R_2 C$  then  $E_2 = \frac{1}{2} CV_s^2$  dissipated in  $R_2$  (independent of  $R_2$ !)

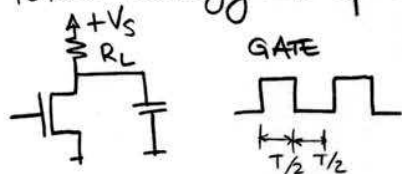Total energy dissipated in  $T = T_1 + T_2$ :  $E = CV_s^2$   $P = \frac{CV_s^2}{T} = CV_s^2 f$




$$\bar{P} = \underbrace{\frac{V_s^2}{2(R_L + R_{ON})}}_{\text{half cycle ON}} + CV_s^2 f \cdot \left( \frac{R_L}{R_L + R_{ON}} \right)^2 \quad R_L \gg R_{ON}$$

$$\bar{P} = \underbrace{\frac{V_s^2}{2R_L}}_{\text{static power}} + \underbrace{CV_s^2 f}_{\text{dynamic power}}$$





# LECTURE 25

## OP-AMPS POSITIVE FEEDBACK

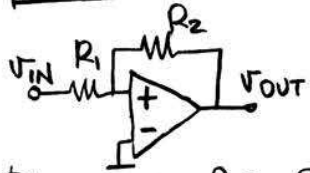

$$V_{OUT} = -\frac{R_2}{R_1} V_{IN} \rightarrow \text{Static analysis, Not enough nor valid now}$$

Dynamics of an Op-Amp

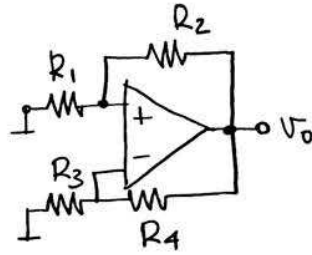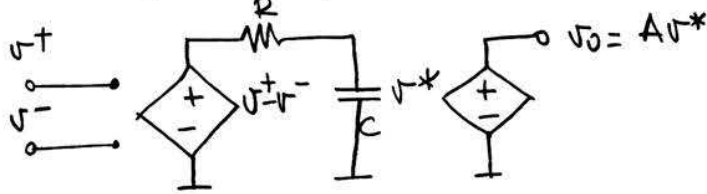

$$\frac{RC}{A} \frac{dv_0}{dt} + \frac{v_0}{A} = v^+ - v^- = \gamma^+ v_0 - \gamma^- v_0$$

$$\gamma^+ = \frac{R_1}{R_2 + R_1}$$

$$\gamma^- = \frac{R_3}{R_3 + R_4}$$

$$\gamma^+ < \gamma^- \text{ STABLE} \quad \gamma^+ > \gamma^- \text{ UNSTABLE} \quad \gamma^+ = \gamma^- \text{ NEUTRAL}$$





$$v_0 = k e^{-t/T}$$

$$T = \frac{RC}{A(\gamma^- - \gamma^+)}$$



> 0 STABLE

< 0 UNSTABLE

Comparator

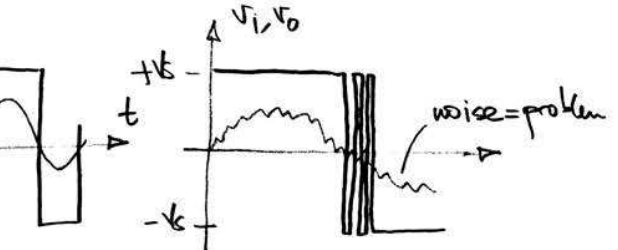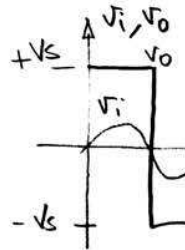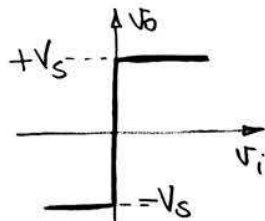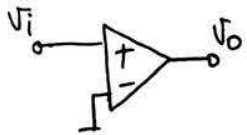


Positive feedback & hysteresis

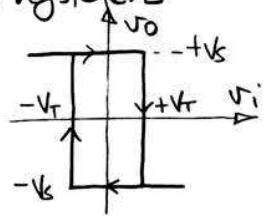
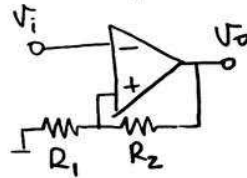


$$V_T = \frac{R_1}{R_1 + R_2} V_S$$

threshold

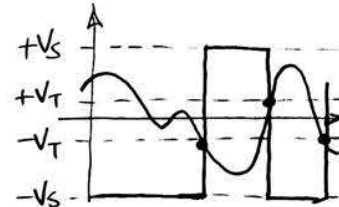

Oscillator

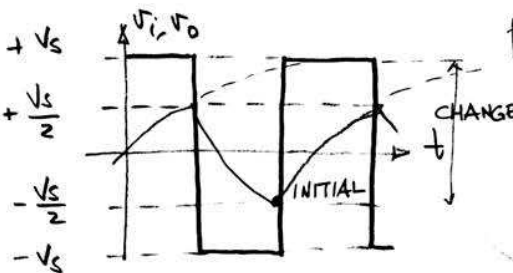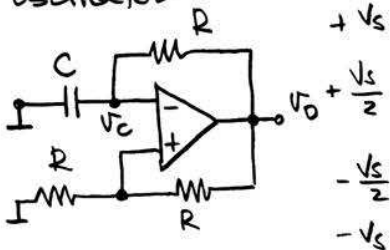

Discretization of time!

When is the signal valid?

$$1 - e^{-tr/RC} = \frac{2}{3} \quad \text{CLOCK HALF CYCLE}$$

$$\frac{tr}{RC} = -\ln \frac{1}{3} = \ln 3$$