

## LECTURES 1, 2 & 3

## LUMPED CIRCUIT ANALYSIS METHODS.

### Method 1:

Kirchhoff Laws

$$\text{KVL} \quad \sum_j V_j = 0$$

$$\text{KCL} \quad \sum_j I_j = 0$$

### Method 2:

Element combination rules

$$\text{SERIES: } R = \sum_j R_j \quad V = \sum_j V_j$$

$$\text{PARALLEL: } G = \sum_j G_j \quad I = \sum_j I_j$$

### Method 3: Node Analysis

1: select ground

2: label other nodes

3: Write KCL for 2:

4: solve for node  $V$

5: solve for branches

### Method 4: Superposition

1: Find responses for each source alone  
(other sources  $V = \text{SHORT}$ ,  $I = \text{OPEN}$ )

2: Sum individual responses

(1 to 5 applied to linear circuits, 1 to 3 applied to any circuit)

### Method 5: Thévenin & Norton

$V_{TH} = v$  measured in OPEN circuit


$I_{NO} = i$  measured in SHORT circuit

$R_{TH} = R_{NO} = r$  measured with all sources OUT

## LECTURE 4

### THE DIGITAL ABSTRACTION

#### STATIC DISCIPLINE

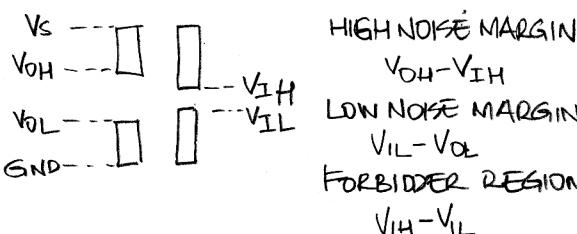


#### BOOLEAN LOGIC

	AND	OR	NOT	NAND	NOR
A B	0 0 0 1 1 0 1 1	0 0 0 1 1 0 1 1	0 1 0 1	0 0 0 1 1 0 1 1	0 1 0 0 1 1 1 0


## LECTURE 5

### INSIDE THE DIGITAL GATE


#### ABSTRACT SWITCH

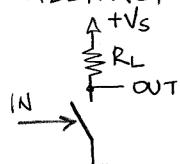

#### MOSFET S-MODEL

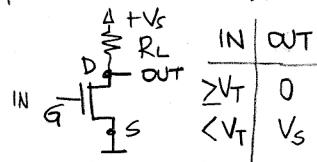
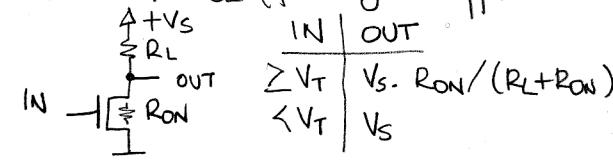
#### MOSFET SR-MODEL (for digital applications)



$$V_T > V_{IL}$$

$$\frac{V_S}{R_{ON} + R_{DS}} < V_{OL}$$

## LECTURE 6 & 7

### NON-LINEAR ANALYSIS & CIRCUITS

#### Method 1:

Analytical

Solve equations

#### Method 2:

Graphical

Draw equations

#### Method 3:

Piecewise linear

Approximate with linear eq.

Small circuit method:

1. find BIAS point

2. Develop linearized circuit

3. Solve linear circuit

#### Incremental Analysis



$$i_D = f(V_D) + \frac{df(V_D)}{dV_D} \cdot \Delta V_D + \dots$$

$$V_D = V_D$$

BIAS POINT


To topology remains. Small signal element equivalence

$$\frac{1}{R} \rightarrow \frac{1}{R}$$

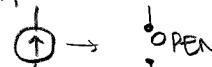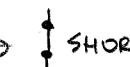

## LECTURE 8


### DEPENDENT SOURCES & AMPLIFIERS

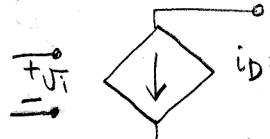

$$i_O = f(i_I)$$

Superposition method  
for dependent sources


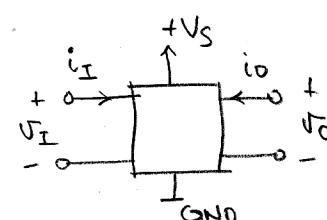
- Leave all dependent sources
- Solve for one independent source at time



$$\frac{\Delta V_O}{\Delta V_I} > 1 \rightarrow \text{Amplification}$$

## LECTURES 9, 10 & 11

## MOSFET SCS MODEL & SATURATION

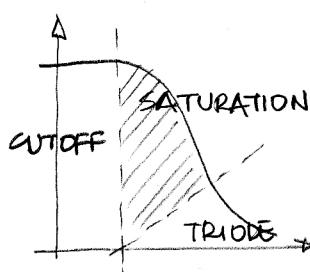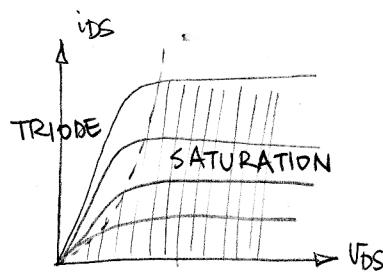


Saturation discipline (analog designs)

$$V_{GS} > V_T$$

$$V_{DS} \geq V_{GS} - V_T$$

$$i_{DS} = \frac{K}{2} (V_{GS} - V_T)^2$$

SMALL SIGNAL

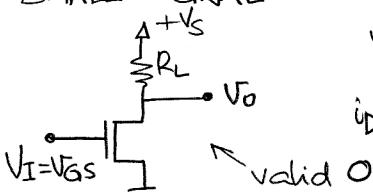

$$\left. \begin{aligned} i_D &= \frac{K}{2} (V_I - V_T) \\ V_O &= V_S - i_D \cdot R_L \end{aligned} \right\} \quad \begin{aligned} V_O &= V_S - \frac{K}{2} (V_I - V_T)^2 \cdot R_L \\ V_O &= -K(V_I - V_T) \cdot R_L \cdot V_I \end{aligned}$$


valid ONLY for this topology

capital O for BIAS

$$V_O = V_S - i_D \cdot R_L$$


$$i_D = \frac{K}{2} (V_I - V_T)$$

gm transconductance

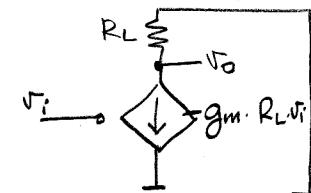

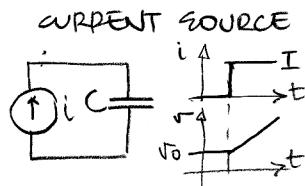
## LECTURES 12 & 13


$$\begin{aligned} i_C &= C \cdot \frac{dV}{dt} \\ V_C &= \frac{1}{C} \int_{-\infty}^t i_C dt \end{aligned}$$



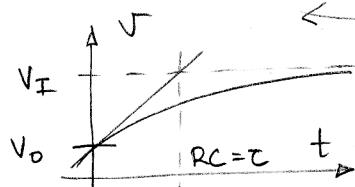
$$\begin{aligned} i &= C \cdot \frac{dV}{dt} \\ V_C &= \frac{V_I - V_O}{R} + C \frac{dV_C}{dt} = 0 \\ RC \frac{dV_C}{dt} + V_C &= V_I \end{aligned}$$



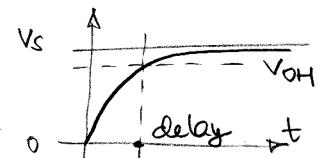
$$V(t) = V_0 e^{-t/RC} + V_I (1 - e^{-t/RC})$$


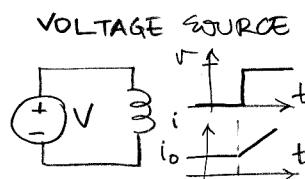
$$\begin{aligned} i_L &= L \frac{di}{dt} \\ V_L &= L \frac{di}{dt} \end{aligned}$$




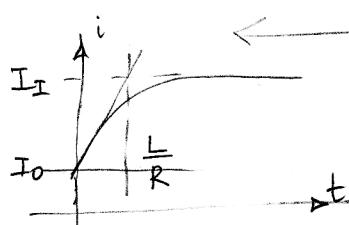
$$\begin{aligned} i &= \frac{1}{L} \int_{-\infty}^t v_L dt \\ V_L &= \frac{V_I - V_O}{R} + \frac{1}{L} \frac{di_L}{dt} = 0 \\ \frac{L}{R} \frac{di_L}{dt} + i_L &= I_2 \end{aligned}$$





$$i(t) = I_0 e^{-Rt/L} + I_2 (1 - e^{-Rt/L})$$

## LECTURE 14

### SPEED OF DIGITAL CIRCUITS

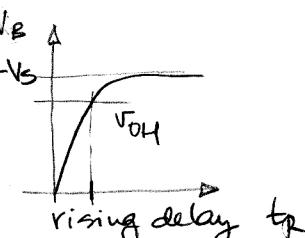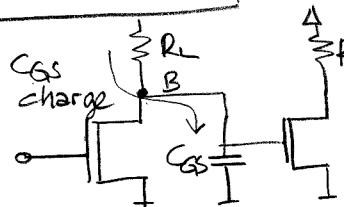

$$V_B = V_S \left( 1 - e^{-t/RLCGS} \right) \Big|_{t=t_r} = V_{OH}$$

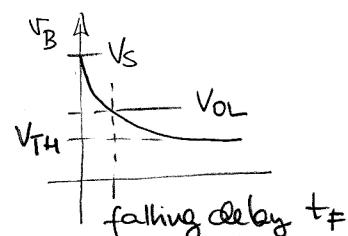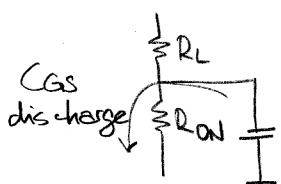


$$V_B = V_{TH} + (V_S - V_{TH}) \cdot e^{-t/R_{TH}CGS}$$

$$V_{TH} = \frac{V_S R_{ON}}{R_L + R_{ON}}$$

$$R_{TH} = \frac{R_L R_{ON}}{R_L + R_{ON}}$$


## LECTURE 15

### RAMPS, STEPS & IMPULSES

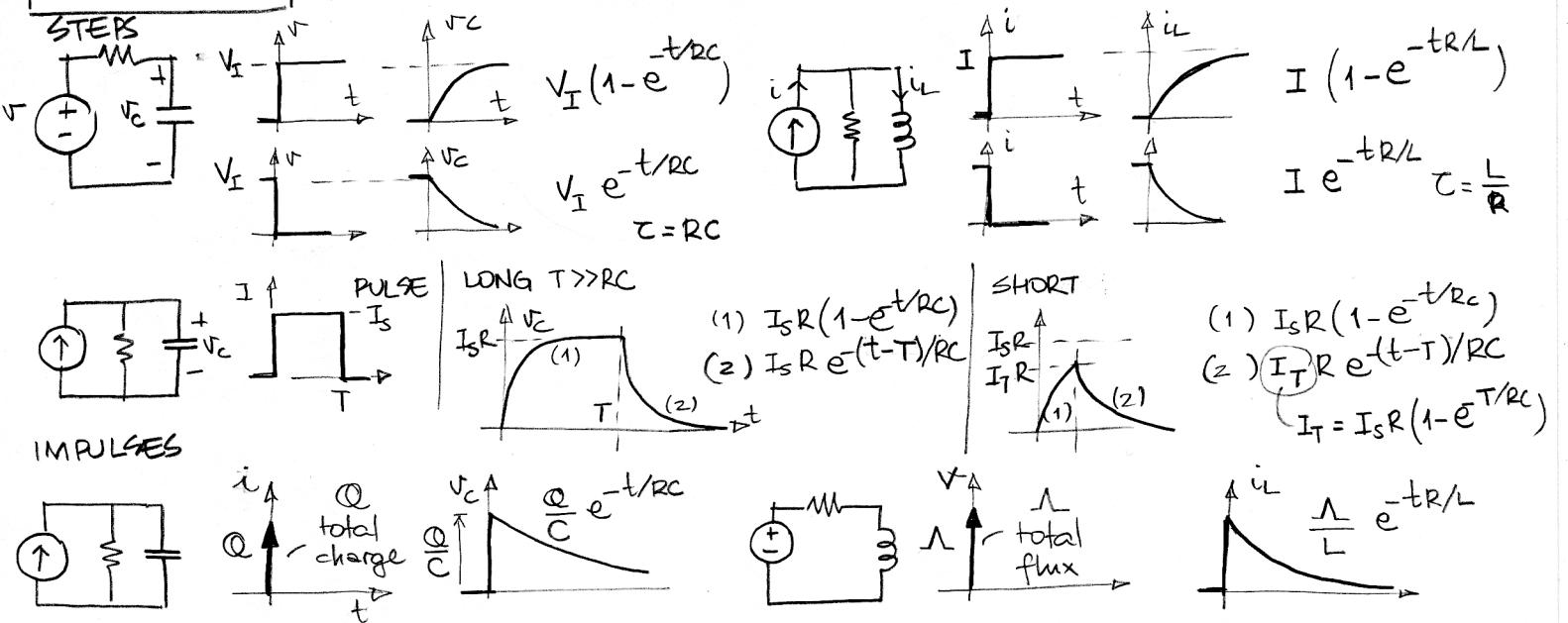


## LECTURE 16

### STATE & MEMORY

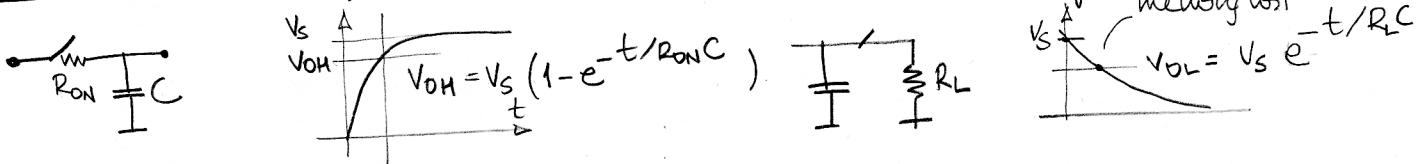


## LECTURE 17 & 18

### SECOND ORDER SYSTEMS

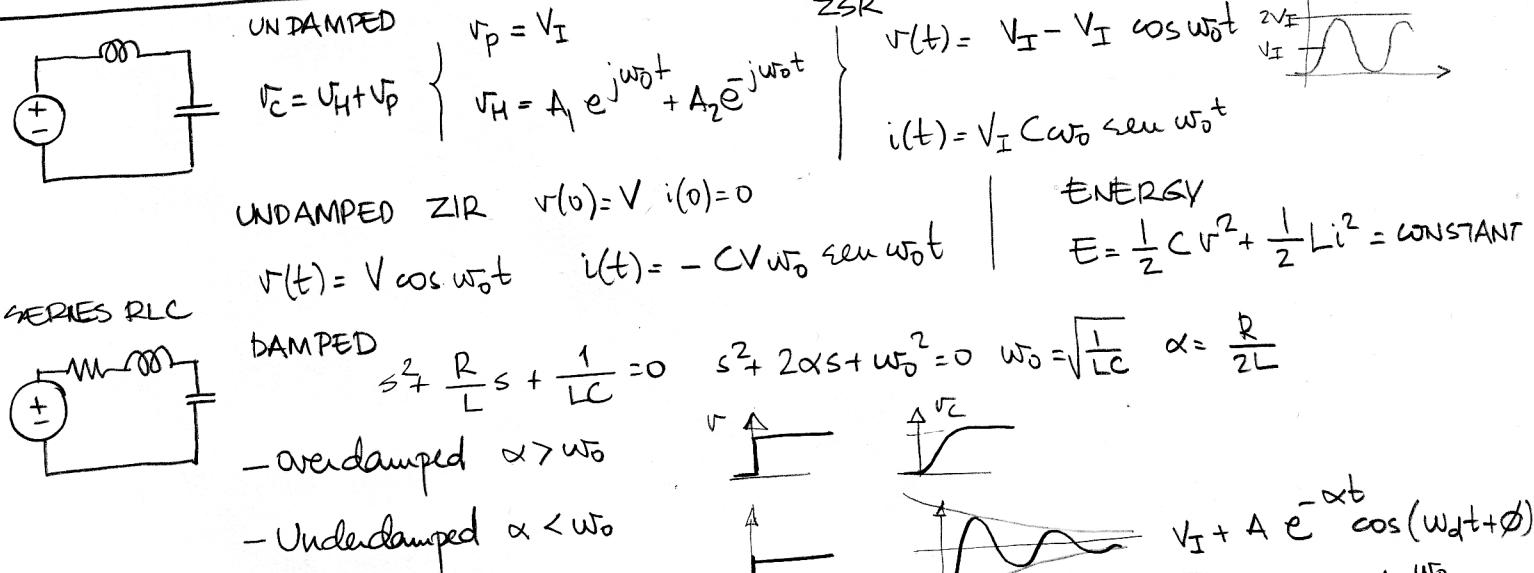

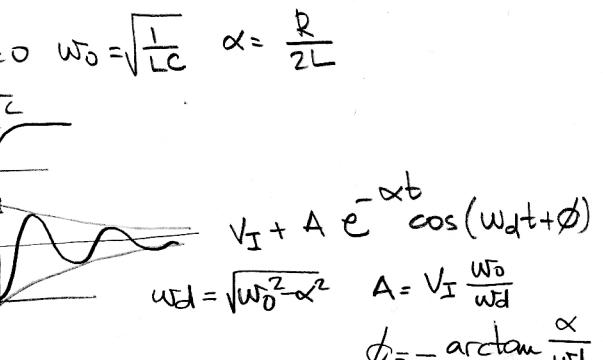
### ENERGY

$$E = \frac{1}{2} C V^2 + \frac{1}{2} L i^2 = \text{CONSTANT}$$



## LECTURE 19


### SINUSOIDAL STEADY STATE

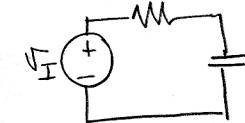

$$V_I = \begin{cases} V_I \cos \omega t & t \geq 0 \\ 0 & t < 0 \end{cases}$$


$$V_C = V_p + V_H = V_p =$$

$\rightarrow$  Steady State

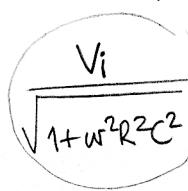

$$= |V_p| = |V_i| \cdot |H(w)|$$

$$\cos(\omega t + \phi)$$

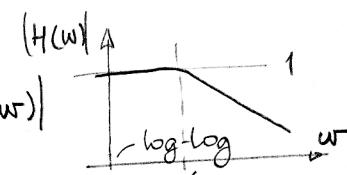

$$\phi = -\arctan(\omega RC) = \angle H(w)$$

## LECTURE 20

## THE IMPEDANCE MODEL

1. Replace sources by complex amplitude
2. Replace elements by impedance
3. Solve circuit
4. Obtain time domain variables

$$-V_i$$

$$Z_R = R$$


$$+V_o$$

$$Z_C = \frac{-j}{\omega C}$$

$$-V_o$$

$$Z_L = j\omega L$$
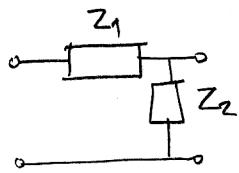
## LECTURE 21 & 22 FILTERS, TIME DOMAIN & FREQUENCY DOMAIN




$$H(\omega) = \frac{Z_2}{Z_1 + Z_2}$$

Second order filters

$$\text{Numerator} \\ s^2 + 2\alpha s t + \omega_0^2$$

$$\Omega = \frac{\omega_0}{2\alpha} \quad \text{quality factor}$$

selectivity

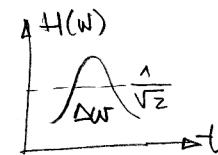


$$\Omega = \frac{\omega_0}{\Delta\omega} \quad \text{bandwidth}$$


number of rings for a step input
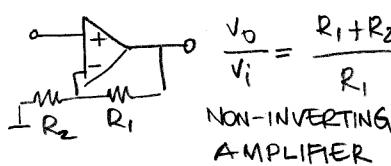
## LECTURES 23, 24 & 25 OPERATIONAL AMPLIFIER


Negative feedback: virtual short/virtual ground




NON-INVERTING AMPLIFIER

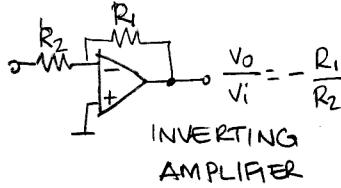


INVERTING AMPLIFIER

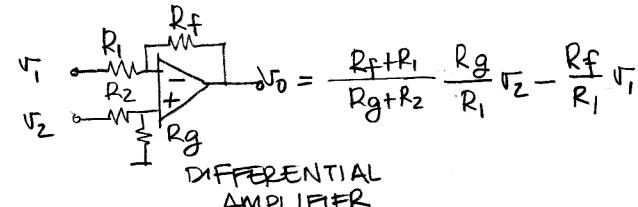

DIFFERENTIAL AMPLIFIER

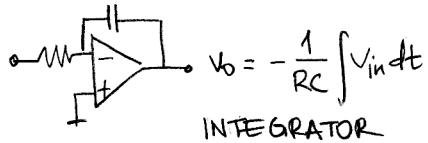

INTEGRATOR

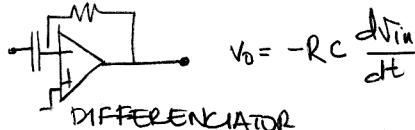


DIFFERENTIATOR

$$\text{IMPEDANCE} \quad \frac{V_o}{V_i} = -\frac{Z_1}{Z_2 + Z_1} e^{j\omega t}$$


+ diode  $i = ae$

Positive feedback

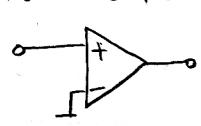

$V_o = -\frac{1}{RC} \int V_{in} dt$


INTEGRATOR

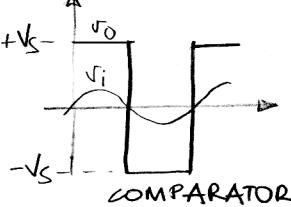


COMPARATOR

$$V_o = -R_C \frac{dV_{in}}{dt}$$

DIFFERENTIATOR

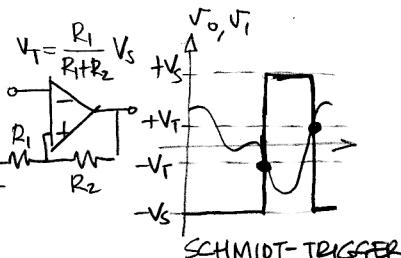

SCHMIDT-TRIGGER

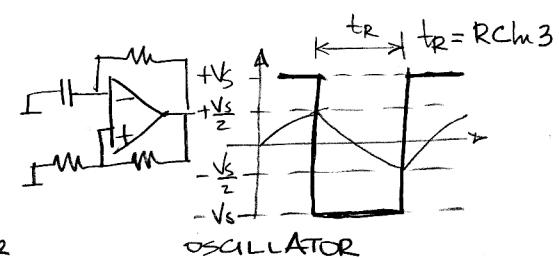

OSCILLATOR

## LECTURES 26 ENERGY & POWER

$$\bar{P} = \left( \frac{V_s^2}{2R_L} \right) + CV_s^2 \cdot f \rightarrow \text{DYNAMIC POWER}$$

STATIC POWER